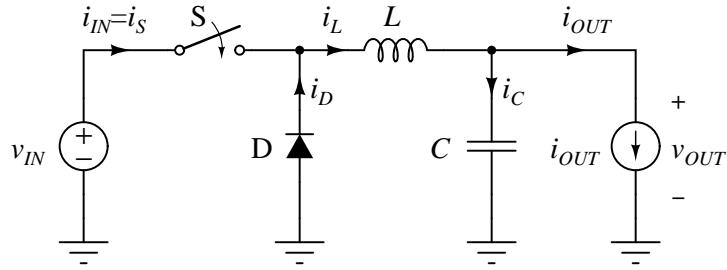



Upravljanje konvertorima



Slika 1: Buck konvertor.

$$\overline{i_S} = \langle i_S \rangle = d i_L$$

$$\overline{v_D} = \langle v_D \rangle = d v_{IN}$$

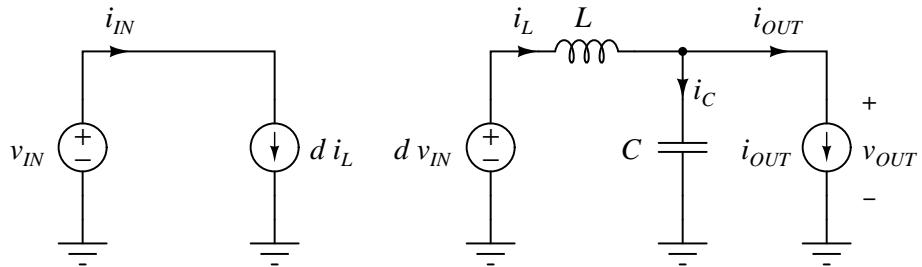

Slika 2: Usrednjeni model buck konvertora.

Sistem jednačina stanja

$$\frac{di_L}{dt} = -\frac{1}{L} v_{OUT} + \frac{1}{L} d v_{IN}$$

$$\frac{dv_{OUT}}{dt} = \frac{1}{C} i_L - \frac{1}{C} i_{OUT}$$

jednačina izlaza (mada je u pitanju ulaz, ali je u sistemu jednačina stanja i_{IN} izlazna promenljiva)

$$i_{IN} = d i_L$$

Nelinearnosti $d v_{IN}$ i $d i_L$

Mali signali, vrednost signala u radnoj tački i odstupanje

$$d = D + \hat{d}$$

$$v_{IN} = V_{IN} + \hat{v}_{IN}$$

$$v_{OUT} = V_{OUT} + \hat{v}_{OUT}$$

$$i_L = I_L + \hat{i}_L$$

$$i_C = I_C + \hat{i}_C = \hat{i}_C$$

$$i_{OUT} = I_{OUT} + \hat{i}_{OUT}$$

$$i_{IN} = I_{IN} + \hat{i}_{IN}$$

Ustaljeno stanje

$$\frac{di_L}{dt} = 0$$

$$\frac{dv_{OUT}}{dt} = 0$$


$$0 = -V_{OUT} + D V_{IN}$$

$$0 = I_L - I_{OUT}$$

$$V_{OUT} = D V_{IN}$$

$$I_{OUT} = I_L$$

Linearizacija

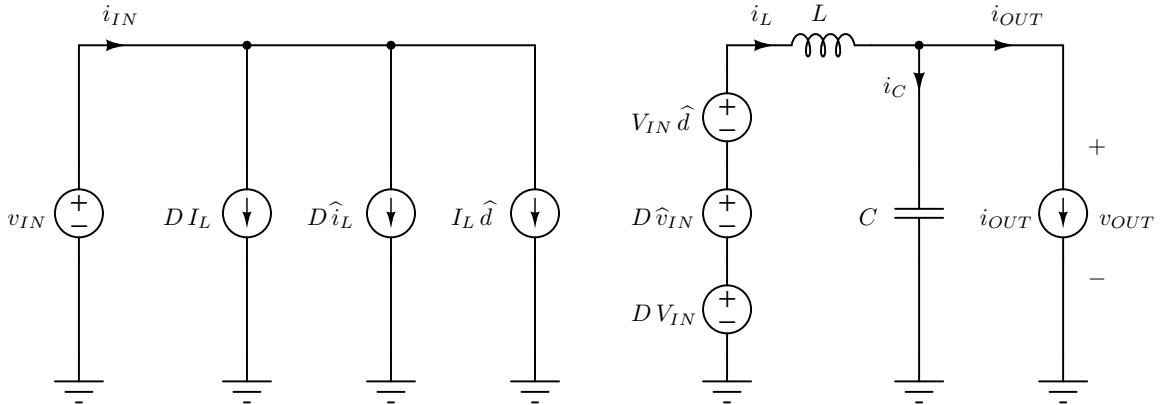

Slika 3: Linearizovan model buck konvertora.

$$d v_{IN} = (D + \hat{d})(V_{IN} + \hat{v}_{IN}) = D V_{IN} + V_{IN} \hat{d} + D \hat{v}_{IN} + \hat{d} \hat{v}_{IN}$$

$$d i_L = (D + \hat{d})(I_L + \hat{i}_L) = D I_L + I_L \hat{d} + D \hat{i}_L + \hat{d} \hat{i}_L$$

$$\hat{d} \hat{v}_{IN} \approx 0$$

$$\hat{d} \hat{i}_L \approx 0$$

$$d v_{IN} \approx D V_{IN} + V_{IN} \hat{d} + D \hat{v}_{IN}$$

$$d i_L \approx D I_L + I_L \hat{d} + D \hat{i}_L$$

linearizovan sistem jednačina stanja

$$\frac{di_L}{dt} = -\frac{1}{L} v_{OUT} + \frac{1}{L} D V_{IN} + \frac{1}{L} V_{IN} \hat{d} + \frac{1}{L} D \hat{v}_{IN}$$

$$\frac{dv_{OUT}}{dt} = \frac{1}{C} i_L - \frac{1}{C} i_{OUT}$$

$$i_{IN} = D I_L + I_L \hat{d} + D \hat{i}_L$$

ili

$$\frac{di_L}{dt} = -\frac{1}{L} v_{OUT} + \frac{1}{L} D v_{IN} + \frac{1}{L} V_{IN} \hat{d}$$

$$\frac{dv_{OUT}}{dt} = \frac{1}{C} i_L - \frac{1}{C} i_{OUT}$$

$$i_{IN} = D i_L + I_L \hat{d}$$


odnosno

$$\frac{d(I_L + \hat{i}_L)}{dt} = -\frac{1}{L} V_{OUT} - \frac{1}{L} \hat{v}_{OUT} + \frac{1}{L} D V_{IN} + \frac{1}{L} D \hat{v}_{IN} + \frac{1}{L} V_{IN} \hat{d}$$

$$\frac{d(V_{OUT} + \hat{v}_{OUT})}{dt} = \frac{1}{C} I_L + \frac{1}{C} \hat{i}_L - \frac{1}{C} I_{OUT} - \frac{1}{C} \hat{i}_{OUT}$$

$$I_{IN} + \hat{i}_{IN} = D I_L + D \hat{i}_L + I_L \hat{d}$$

Primenom teoreme superpozicije

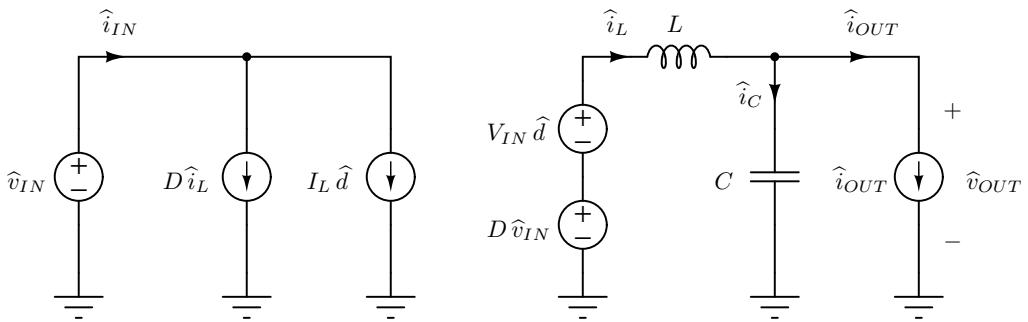

Slika 4: Linearizovan model za male signale buck konvertora.

$$\frac{d\hat{i}_L}{dt} = -\frac{1}{L} \hat{v}_{OUT} + \frac{1}{L} D \hat{v}_{IN} + \frac{1}{L} V_{IN} \hat{d}$$

$$\frac{d\hat{v}_{OUT}}{dt} = \frac{1}{C} \hat{i}_L - \frac{1}{C} \hat{i}_{OUT}$$

jednačina izlaza

$$\hat{i}_{IN} = D \hat{i}_L + I_L \hat{d}$$

sada je sistem linearan

Prenosne funkcije:

$$H_1(s) = \frac{\hat{v}_{OUT}(s)}{\hat{d}(s)} = \frac{V_{IN}}{1 + s^2LC}$$

$$H_2(s) = \frac{\hat{v}_{OUT}(s)}{\hat{v}_{IN}(s)} = \frac{D}{1 + s^2LC}$$

$$H_3(s) = \frac{\hat{v}_{OUT}(s)}{\hat{i}_{OUT}(s)} = -\frac{sL}{1 + s^2LC}$$